

Assignment#1

Q1.) For the transmission gate, derive graphically the transfer characteristics (V_{out} versus V_{in}), and I_d versus V_{in} with (W/L) of NMOS transistor as 2:1 and the (W/L) of PMOS as 4:1. Assume 45 nm and 22 nm technology node model file. Use LT Spice tool to derive the characteristics. Plot readable graphs showing transfer characteristics (V_{out} versus V_{in}), and I_d versus V_{in} . V_{in} can range from 0 to 5V, in steps of 0.5 V.

Also use the long channel current model expression, and determine the transfer characteristics (V_{out} versus V_{in}), and I_d versus V_{in} , and plot readable graphs manually either by using hand-calculations or by Matlab/Python. V_{in} can range from 0 to 5V, in steps of 0.5 V. You may use Matlab/Python to find the solutions for a lengthy expression.

Q2.) Draw a plot showing C-V characteristics of an NMOS transistor. Consider NMOS transistor of 45 nm and 22 nm technology node for a channel length of 1 micron, width of 360 nm using LT Spice. (Note that C-V graph should not be a print-screen of LTSpice, but rather a readable plot of the data captured from LTSpice).